

# Design of Control Path

*Debdeep Mukhopadhyay*

# Hardwired Hardware

# GCD Processor

```
gcd(in: X, Y; out: Z);  
  register XR, YR, TEMPR;  
  XR := X;                                { Input the data }  
  YR := Y;  
  while XR > 0 do begin  
    if XR ≤ YR then begin                  { Swap XR and YR }  
      TEMPR := YR;  
      YR := XR;  
      XR := TEMPR; end  
      XR := XR − YR;                      { Subtract YR from XR }  
    end  
    Z := YR;                              { Output the result }  
  end gcd;
```

---


**Figure 5.5**

Procedure *gcd* to compute the greatest common divisor of two numbers.

# An Example

Conditions		Actions	
		$XR := 20; YR := 12;$	
$XR > 0:$	$XR > YR:$	$XR := XR - YR = 8;$	
$XR > 0:$	$XR \leq YR:$	$YR := 8; XR := 12;$	$XR := XR - YR = 4;$
$XR > 0:$	$XR \leq YR:$	$YR := 4; XR := 8;$	$XR := XR - YR = 4;$
$XR > 0$	$XR \leq YR:$	$YR := 4; XR := 4;$	$XR := XR - YR = 0;$
$XR \leq 0:$		$Z := 4;$	

# Hardware for the GCD processor

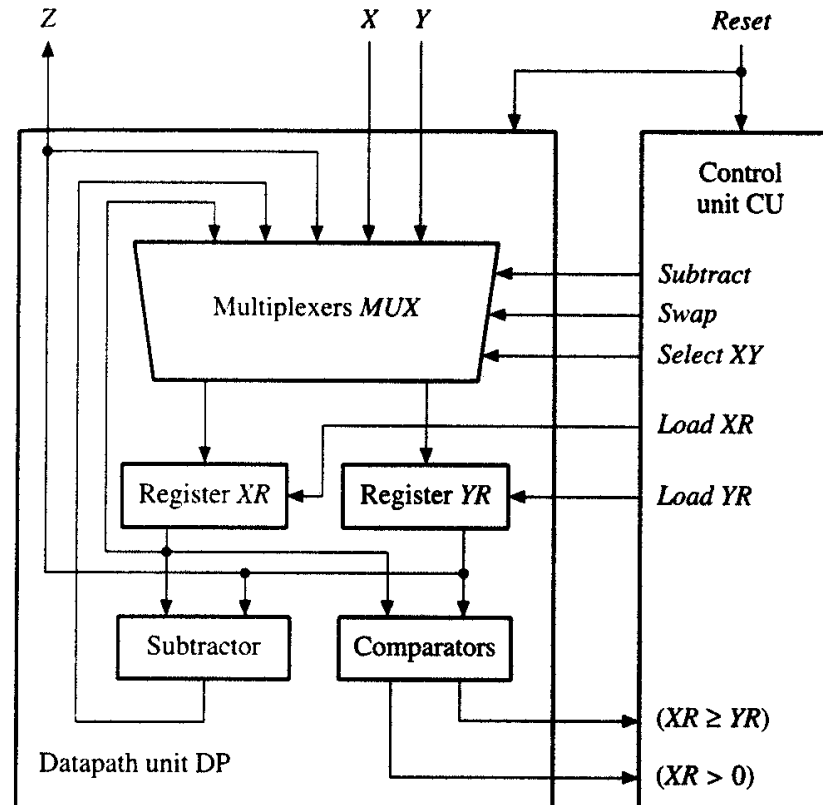

# State Table for the Control Unit

State	Inputs ( $XR > 0$ ) ( $XR \geq YR$ )			Outputs				
	0–	10	11	<i>Subtract</i>	<i>Swap</i>	<i>Select XY</i>	<i>Load XR</i>	<i>Load YR</i>
$S_0$ (Begin)	$S_3$	$S_1$	$S_2$	0	0	1	1	1
$S_1$ (Swap)	$S_2$	$S_2$	$S_2$	0	1	0	1	1
$S_2$ (Subtract)	$S_3$	$S_1$	$S_2$	1	0	0	1	0
$S_3$ (End)	$S_3$	$S_3$	$S_3$	0	0	0	0	0


What kind of state machine is this?

# Classical method

$S_0 = 00$ ,  $S_1 = 01$ ,  $S_2 = 10$  and  $S_3 = 11$

Inputs		Present state		Next state		Outputs				
$(XR > 0)$	$(XR \geq YR)$	$D_1$	$D_0$	$D_1^+$	$D_0^+$	<i>Subtract</i>	<i>Swap</i>	<i>Select XY</i>	<i>Load XR</i>	<i>Load YR</i>
0	<i>d</i>	0	0	1	1	0	0	1	1	1
0	<i>d</i>	0	1	1	0	0	1	0	1	1
0	<i>d</i>	1	0	1	1	1	0	0	1	0
0	<i>d</i>	1	1	1	1	0	0	0	0	0
1	0	0	0	0	1	0	0	1	1	1
1	0	0	1	1	0	0	1	0	1	1
1	0	1	0	0	1	1	0	0	1	0
1	0	1	1	1	1	0	0	0	0	0
1	1	0	0	1	0	0	0	1	1	1
1	1	0	1	1	0	0	1	0	1	1
1	1	1	0	1	0	1	0	0	1	0
1	1	1	1	1	1	0	0	0	0	0

Excitation Table

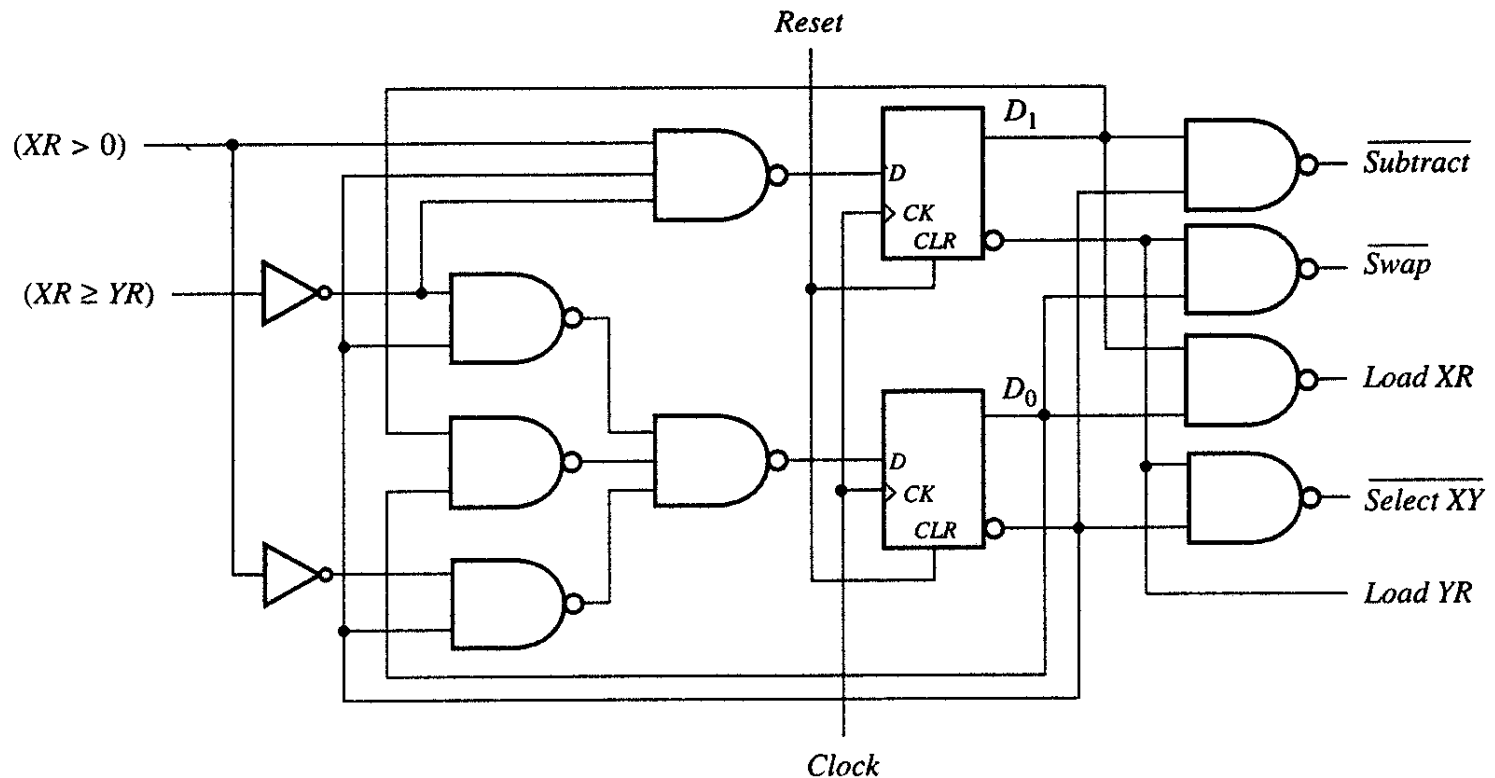

**Is this a Moore or Mealy Machine?**



# Design based on Microprogram

# Concept of Microprogram

- High Level description of a double precision ADD:
  - ADD AL, BL
  - ADDC AH, BH
- Low level description: Microprogram

Cycle	Function Select	Storage Control	Data Routing
1	Add	Read AL, Read BL, Write AL	...
2	Add with carry	ReadAH, Read BH, Write AH	...

# What is a Microprogram?

## **Microprogram**

- **Program stored in memory that generates all the control signals required to execute the instruction set correctly**
- **Consists of microinstructions**

## **Microinstruction**

- **Contains a control word and a sequencing word**
  - Control Word - All the control information required for one clock cycle**
  - Sequencing Word - Information needed to decide the next microinstruction address**


## **Control Memory(Control Storage: CS)**

- **Storage in the microprogrammed control unit to store the microprogram**


# What is a Microprogram?

- *Microprogramming* is so named because it uses concepts from regular *programming*. The *micro* prefix should remind you, however, that the microprogram used by a processor is different from the program executed by the processor.
- The main thing to remember is that we have a computer inside a computer, but that the inner computer is much simpler and more restricted


# Micro-programmed Control Unit

 

(a)

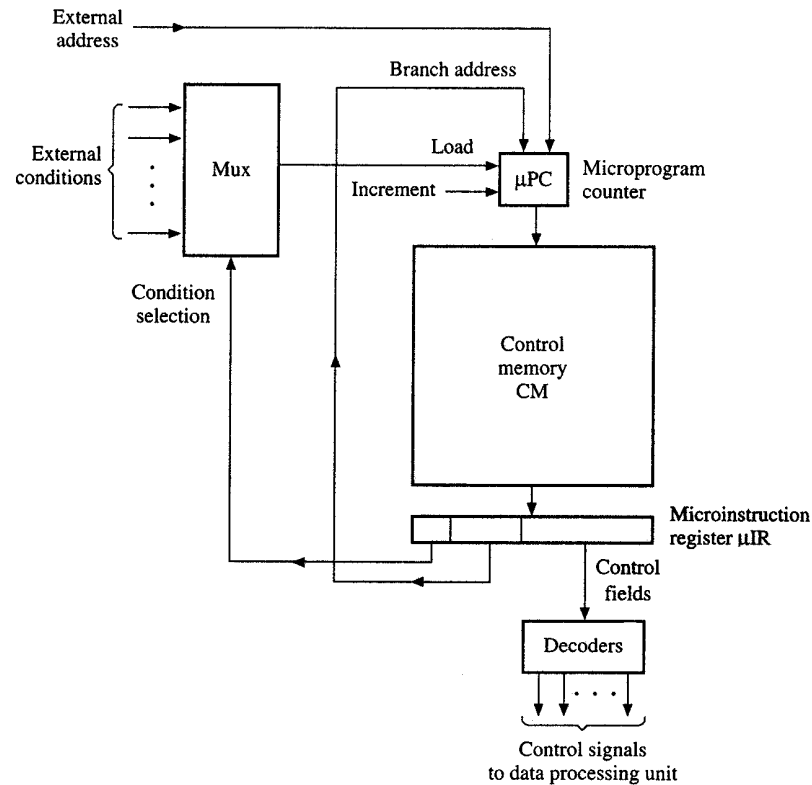

# Symbolic Micro-program

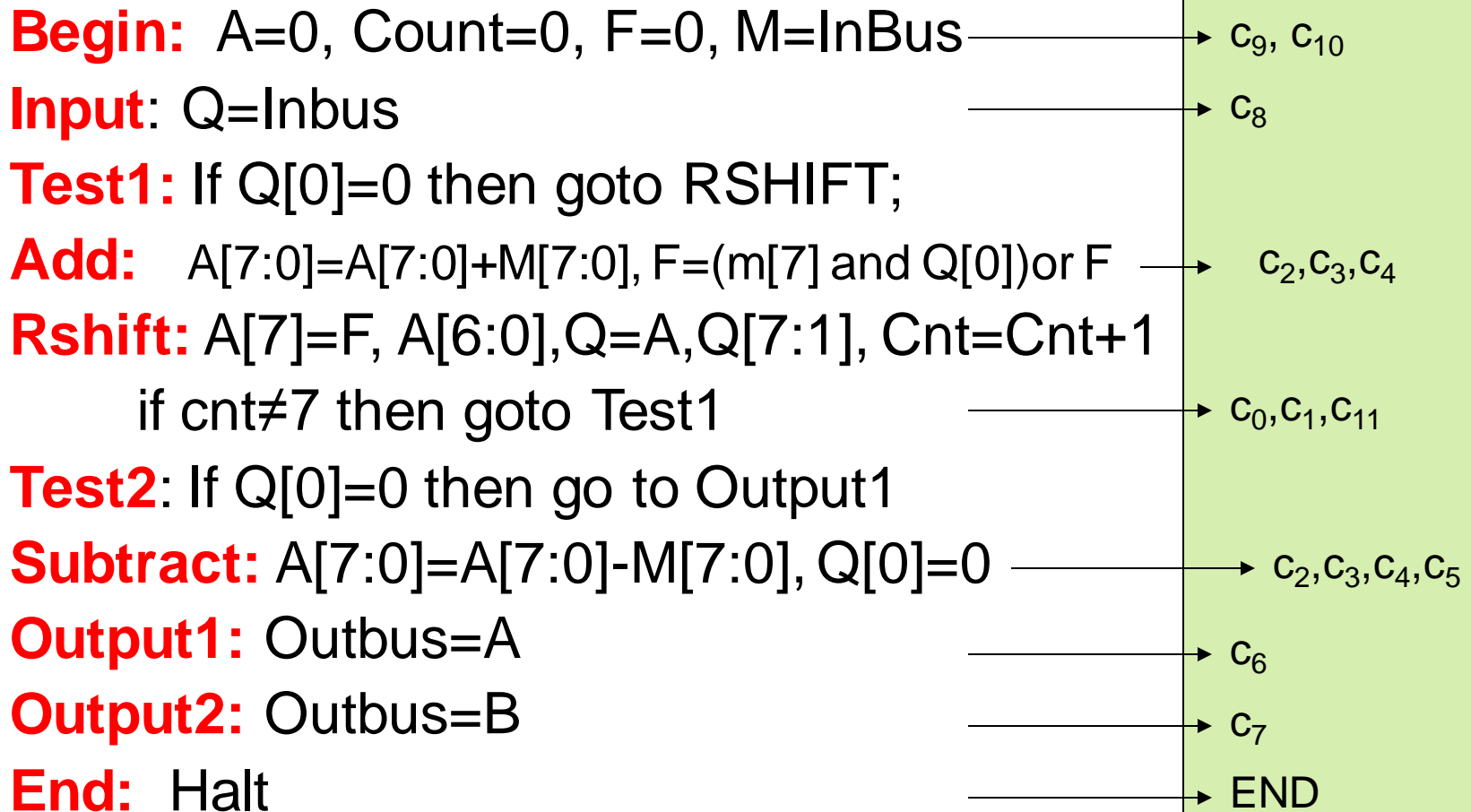

# Control Signals

---

Control Signal	Operation controlled
$c_0$	Set sign bit of A to F.
$c_1$	Right-shift register-pair A.Q.
$c_2$	Transfer adder output to A.
$c_3$	Transfer A to left input of adder.
$c_4$	Transfer M to right input of adder.
$c_5$	Perform subtraction (correction). Clear Q[0].
$c_6$	Transfer A to output bus.
$c_7$	Transfer Q to output bus.
$c_8$	Transfer word on input bus to Q.
$c_9$	Transfer word on input bus to M.
$c_{10}$	Clear A, COUNT, and F registers.
$c_{11}$	Increment COUNT.
END	Completion signal (CU idle).

---

# Branching

*No Branching*

*Branch if  $Q[0]=0$*

*Branch if  $\text{Count} \neq 7$*

*Unconditional Branch*

Hence a 2-bit conditional select field is needed.


There are 10 states, so 4 bits are enough to encode the states.




# Binary Microprogram

[illegible]

# Control Path Design

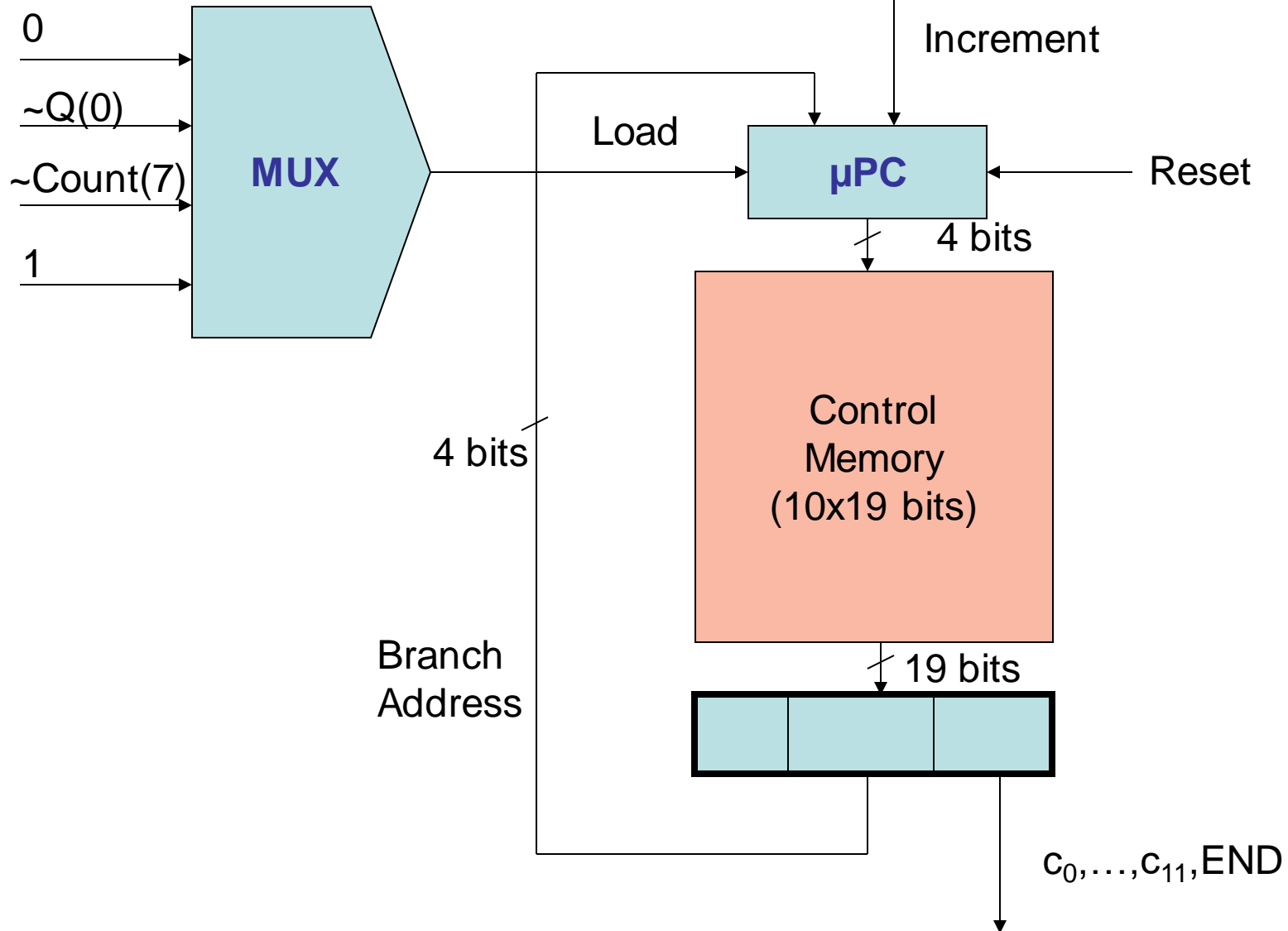

# Data Path Design

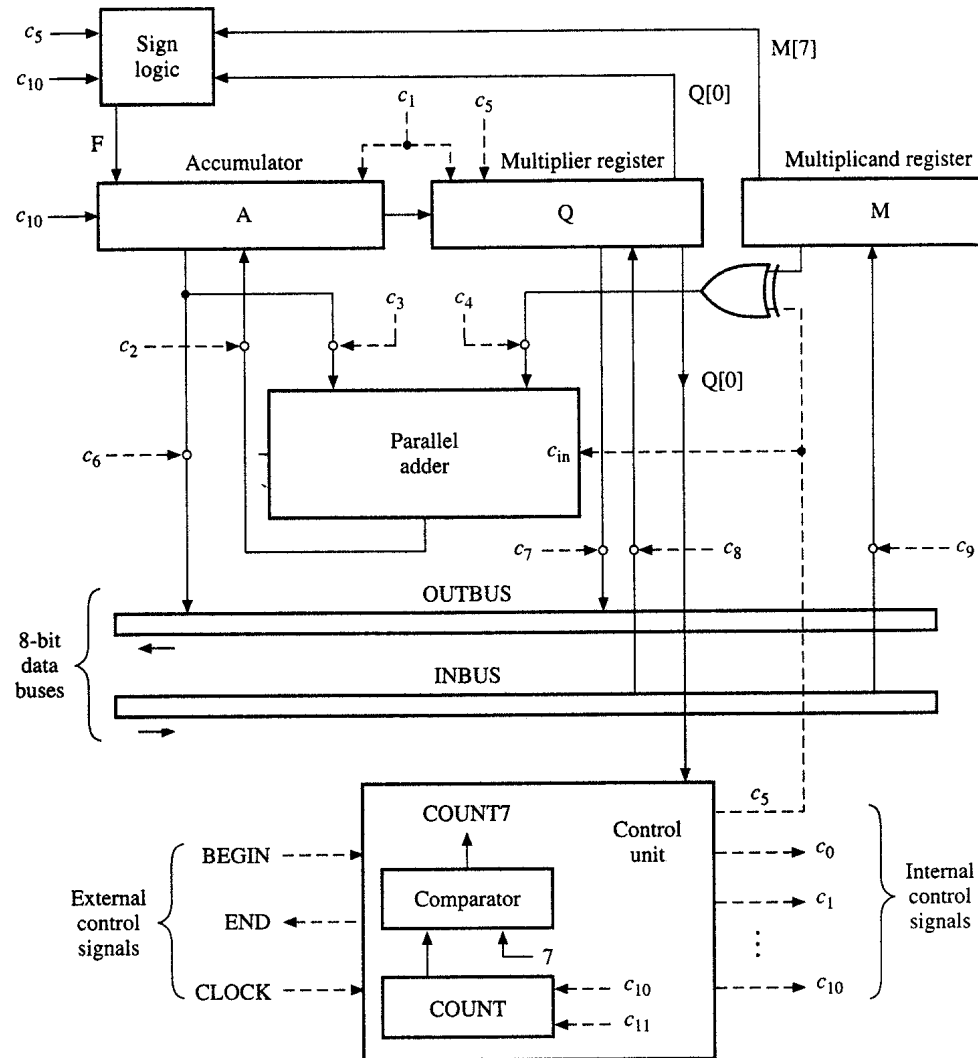

# Comments

- Micro-programming helps in making Control Units which may be changed by changing the content of the memory.
- But slow due to the fetch timing of the instruction from the memory.

# Assignment 2

1. Write a verilog code to implement the control path for a gcd processor.
2. Write a verilog code to implement the micro-programmed control unit of a 2's complement signed fraction multiplier.

Deadline: 21/3/08