

Modeling Combinational Logic Circuits

Debdeep Mukhopadhyay

Types

1. logical/ arithmetical equations
2. multiplexers
3. encoders
4. priority encoders
5. decoders
6. comparators
7. Arithmetic Logic Units (ALUs)

Useful Verilog Constructs


- if
- case
 - casex: handles don't cares also.
- for: leads to compact coding.
- always
- assign

Use of parenthesis

- `module logic_struct(A1,B1,C1,D1,A2,B2,C2,D2,Y1,Y2);`

 output [7:0] Y1,Y2;
 reg [7:0] Y1,Y2;
 always @(A1 or B1 or C1 or D1 or A2 or B2 or C2 or
D2)
 begin
 Y1=A1+B1+C1+D1;
 Y2=(A2+B2)+(C2+D2);
 end
 end
`endmodule`

Synthesized Circuit Structure

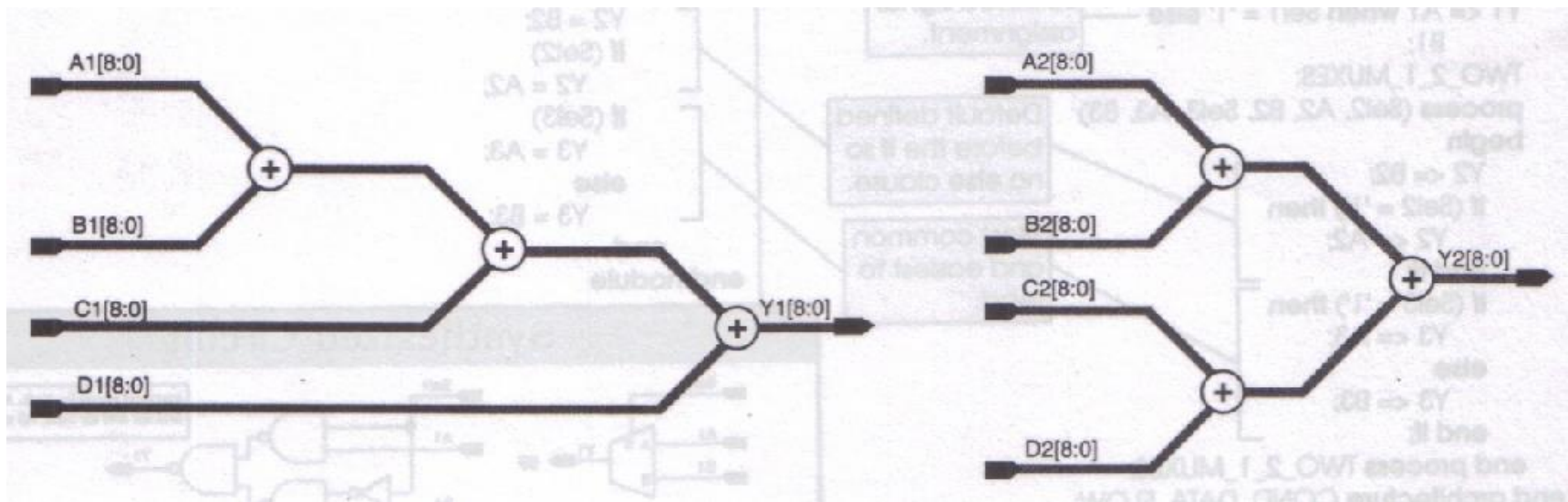


Second circuit has a shorter critical delay (longest path delay)!

Modeling Multiplexers

- Five ways of modeling multiplexers:
 - one if statement with multiple else/else if clauses.
 - nested if statements
 - case statements

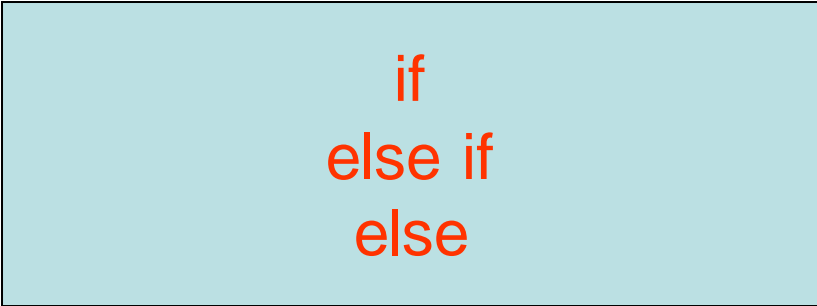4-1 Mux: method 1

```
always @(sel or A or B or C or D)
begin
    if(sel==2'b0)
        Y=A;
    else if(sel==2'b01)
        Y=B;
    else if(sel==2'b10)
        Y=C;
    else
        Y=D;
```



if
else if
else

4-1 Mux: method 2

- always @(sel or A or B or C or D)

```
if(sel[1]==0)
    if(sel[0]==0)
        Y=A; //sel=00
    else
        Y=B; //sel=01
else
    if(sel[0]==0)
        Y=C; //sel=10
    else
        Y=D; //sel=11
```

nested if, else statements

4-1 Mux: method 3

- always @(sel or A or B or C or D)
 case(sel)
 2'b00: Y=A;
 2'b01: Y=B;
 2'b10: Y=C;
 2'b11: Y=D;
 default: Y=A;
 endcase

More Compact and clear

A Comparison: Case is simulation efficient

Sparc/32Mb RAM, Solaris 2.5, Verilog XL	Data Structure (bytes of memory)	Memory Usage Percentages	Simulation Time (in seconds)	CPU Simulation
CaseMux8	92252	100.00%	1209.3	100%
Ifmux8	92912	100.72%	1282.0	106.01%

Encoders

- Discrete quantities of digital data are often represented in a coded form.
- Encoders do that.
- A typical encoder takes in 2^n input lines and provides n encoded output lines.
- Assume that only one of the inputs is 1 at any given time, otherwise the output is undefined and have some meaningless value.

8-3 encoder

[illegible]

Verilog code

```
always @(A)
begin
  if(A==8'b00000001) Y=0;
  else if(A==8'b00000010)Y=1;
  else if(A==8'b00000100)Y=2;
  ...
  else if(A==8'b10000000)Y=7;
  else Y=3'bx;
end
```

Why is this
line kept?

Verilog code

```
always @(A)
begin
  if(A==8'b00000001) Y=0;
  else if(A==8'b00000010)Y=1;
  else if(A==8'b00000100)Y=2;
  ...
  else if(A==8'b10000000)Y=7;
  else Y=3'bx;
end
```

Minimizes the synthesizer circuit.
The synthesizer may take for the 256-8
input cases
specified, the output as 0 or 1 as per
required, to generate a small circuit.

Using casex

- ```
always @(A)
begin
 casex(A)
 8'b 00000001: Y=0;
 8'b 00000010: Y=1;
 8'b 00000100: Y=2;
 ...
 8'b 10000000: Y=7;
 default: Y=3'bx;
 endcase
end
```

# Using for loop

- always @(A)  
begin  
    Test=8'b00000001;  
    Y=3'bx;  
    for(N=0;N<8;N=N+1)  
        begin  
            if(A==Test)  
                Y=N;  
            Test=Test<<1;  
        end  
    end  
end

*Compact and does not  
grow with dimensions!*



# Priority Encoders

- Operation of Priority encoder is such that if two or more single bit inputs are at logic 1, then the input with highest priority will take precedence.
- How to code in verilog?

# Model 1

```
always @(A)
begin
 Valid=1;
 if(A[7]) Y=7;
 else if(A[6]) Y=6;
 else if(A[5]) Y=5;
 ...
 else if(A[0]) Y=0;
 else
 begin
 Valid=0
 Y=3'bx;
 end
 end
end
```

# Model 2

```
always@(A)
begin
 Valid=1;
 casex(A)
 8'b1xxxxxxx: Y=7;
 8'b01xxxxxx: Y=6;
 ...
 8'b00000001: Y=0;
 default: begin
 Valid=0;
 Y=3'bx;
 end
 endcase
end
```

# Model 3


```
always @(A)
begin
 Valid=0;
 Y=3'bx;
 for(N=0;N<8;N=N+1)
 if(A[N])
 begin
 Valid=1;
 Y=N;
 end
 end
end
```

# Decoders

- Decode data that has been previously encoded using possibly binary format.
- Automatic priority encoding with if and case, and “don’t care” output values are not needed.
- The codes are left as an exercise.

# Assignment 1

 - **Problem 1:** Write a verilog code for a four bit address decoder. It provides enable signals for segments of memory, the address map of which is shown below.



# Assignment1

- **Problem 2:**

Design a generic  $n$ -bit input,  $m$ -bit output binary decoder, with a separate enable input.

Instantiate the written module from another module, to realize a  $(2,4)$  and  $(3,6)$  decoder.

# Assignment1

- **Problem 3:** Compare the if else, nested if, case and for coding styles for modeling of various combinational blocks in terms of simulation time, cpu utilization and memory utilization of the processor. You can add any other interesting metric of your choice.