

# Hardware Description Language (HDL)


The first step of the Design Flow

**D. Mukhopadhyay**

**Dept of Computer Sc and Engg,**


**`debdeep@cse.iitkgp.ernet.in`**

# How it started!

 


- Gateway Design Automation
- Cadence purchased Gateway in 1989.
- Verilog was placed in the public domain.
- Open Verilog International (OVI) was created to develop the Verilog Language as IEEE standard.

# The Verilog Language

 


- Originally a modeling language for a very efficient event-driven digital logic simulator
- Later pushed into use as a specification language for logic synthesis
- Now, one of the two most commonly-used languages in digital hardware design (VHDL is the other)
- Virtually every chip (FPGA, ASIC, etc.) is designed in part using one of these two languages
- Combines structural and behavioral modeling styles

# Concurrency

 


- Verilog or any HDL has to have the power to model concurrency which is natural to a piece of hardware.
- There may be pieces of two hardware which are even independent of each other.
- Verilog gives the following constructs for concurrency:
  - always
  - assign
  - module instantiation
  - non-blocking assignments inside a sequential block

# However...

 


- The simulating machine is sequential.
- no-matter how many processors I have, I can write one more process which also have to be simulated concurrently.
- So, the processes are scheduled sequentially so that we have a feeling of parallelism:
  - like the desktop of our PC where we may open an editor, a netscape and so on. We have a feeling that they are executed parallely, but in reality there is a serialization involved.

# Race...

 


- So, always blocks (for example) are parallel...
- Even though they are not actually.
- So, which always block gets executed first? My simulation results will depend upon that!
- Standards do not say anything.
- It may be that the last always block is executed first...
- and so we have race!

# How do we overcome race?

 

- We shall see in the class...
- Try to think of a clean hardware and you will not have race

# Multiplexer Built From Primitives

 

```
module mux(f, a, b, sel);
```

← Verilog programs built from modules

```
output f;
```


← Each module has an interface

```
input a, b, sel;
```

```
and    g1(f1, a, nsel),  
      g2(f2, b, sel);  
or     g3(f, f1, f2);  
not    g4(nsel, sel);
```


Module may contain structure: instances of primitives and other modules

```
endmodule
```

 




# Multiplexer Built From Primitives

 


```
module mux(f, a, b, sel);  
output f;  
input a, b, sel;
```

Identifiers not  
explicitly defined  
default to wires
 
```
and    g1(f1, a, nsel),  
      g2(f2, b, sel);  
or     g3(f, f1, f2);  
not    g4(nsel, sel);  
  
endmodule
```



# Multiplexer Built With Always

 


```
module mux(f, a, b, sel);  
output f;  
input a, b, sel;  
reg f;
```

Modules may contain one or more *always* blocks


```
always @(a or b or sel)  
  if (sel) f = b;  
  else f = a;
```

Sensitivity list contains signals whose change triggers the execution of the block

```
endmodule
```

 

# Multiplexer Built With Always

 


```
module mux(f, a, b, sel);  
output f;  
input a, b, sel;  
reg f;
```

A *reg* behaves like memory:  
holds its value until  
imperatively assigned  
otherwise


```
always @(a or b or sel)  
if (sel) f = b;  
else f = a;
```

Body of an *always*  
block contains  
traditional imperative  
code

```
endmodule
```

 


# Mux with Continuous Assignment

 


```
module mux(f, a, b, sel);  
output f;  
input a, b, sel;  
  
assign f = sel ? b : a;  
  
endmodule
```

LHS is always set to the value on the RHS

 Any change on the right causes re-evaluation




# Identifiers in Verilog

 


- Any Sequence of letter, digits, dollar sign, underscore.
- First character must be a letter or underscore.
- It cannot be a dollar sign.
- Cannot use characters such as hyphen, brackets, or # in verilog names

# Verilog Logic Values

 


- Predefined logic value system or value set : '0', '1', 'x' and 'z';
- 'x' means uninitialized or unknown logic value
- 'z' means high impedance value.

# Verilog Data Types

 

- Nets: wire, supply1, supply0
  - wire:
    - i) Analogous to a wire in an ASIC.
    - ii) Cannot store or hold a value.
- Integer: used for the index variables of say for loops. No hardware implication.


# The reg Data Type

 

- Register Data Type: Comparable to a variable in a programming language.
- Default initial value: 'x'
- ```
module reg_ex1;  
  reg Q; wire D;  
  always @(posedge clk) Q=D;
```
- A reg is not always equivalent to a hardware register, flipflop or latch.
- ```
module reg_ex2; // purely combinational  
  reg c;  
  always @(a or b) c=a|b;  
endmodule
```



 
# Difference between driving and assigning



- Programming languages provide variables that can contain arbitrary values of a particular type.
- They are implemented as simple memory locations.
- Assigning to these variables is the simple process of storing a value into the memory location.
- Verilog reg operates in the same way. Previous assignments have no effect on the final result.

# Example

 

- module assignments;  
reg R;  
initial R<=#20 3;  
initial begin  
    R=5; R=#35 2;  
end  
initial begin  
    R<=#100 1;  
    #15 R=4;  
    #220;  
    R=0;  
end  
endmodule


The variable R is shared by all the concurrent blocks.

R takes the value that was last assigned.

This is like a hardware register which also stores the value that was last loaded into them.


***But a reg is not necessarily a hardware register.***

# Wire: helps to connect

 

- Consider a set of tristate drivers connected to a common bus.
- The output of the wire depends on *all* the outputs and not on the last one.
- To model connectivity, any value driven by a device must be driven continuously onto that wire, in parallel with the other driving values.

# Code

 


- ```
module simple(A,B,C,sel,Z);  
  input A, B, C;  
  input [1:0] sel;  
  output Z;  
  reg Z;  
  always @(A or B or C or SEL)  
  begin  
    2'b00: Z=1'bz;  
    2'b01: Z=A;  
    2'b10: Z=B;  
    2'b11: Z=C;  
  endcase  
end  
endmodule
```

- ```
module simple(A,B,C,sel,Z);  
  input A, B, C;  
  input [1:0] sel;  
  output Z;  
  
  assign Z=(SEL==2'b01)?A: 1'bz;  
  assign Z=(SEL==2'b10)?B: 1'bz;  
  assign Z=(SEL==2'b11)?C: 1'bz;  
  
endmodule
```


Inferred as a multiplexer.  
But we wanted drivers!

# Numbers

 


- Format of integer constants:  
Width' radix value;
- Verilog keeps track of the sign if it is assigned to an integer or assigned to a parameter.
- Once verilog loses sign the designer has to be careful.

# Hierarchy

 

- Module interface provides the means to interconnect two verilog modules.
- Note that a reg cannot be an input/ inout port.
- A module may instantiate other modules.

# Instantiating a Module

 

- Instances of


```
module mymod(y, a, b);
```

- Lets **instantiate** the module,

```
mymod mm1(y1, a1, b1); // Connect-by-position
```

```
mymod mm2(.a(a2), .b(b2), .y(c2)); // Connect-by-name
```


# Sequential Blocks

 

- Sequential block is a group of statements between a begin and an end.
- A sequential block, in an always statement executes repeatedly.
- Inside an initial statement, it operates only once.




# Procedures

 

- A Procedure is an always or initial statement or a function.
- Procedural statements within a sequential block executes concurrently with other procedures.

# Assignments

 


- module assignments  
// continuous assignments  
always // beginning of a procedure  
begin //beginning of a sequential block  
//....Procedural assignments  
end  
endmodule
- A Continuous assignment assigns a value to a wire like a real gate driving a wire.

```
module holiday_1(sat, sun, weekend);  
  input sat, sun; output weekend;  
  // Continuous assignment  
  assign weekend = sat | sun;  
endmodule
```


```
module holiday_2(sat, sun, weekend);  
  input sat, sun; output weekend;  
  reg weekend;  
  always @(sat or sun)  
    weekend = sat | sun; // Procedural  
endmodule // assignment
```

# Blocking and Nonblocking Assignments

 

- Blocking procedural assignments must be executed before the procedural flow can pass to the subsequent statement.
- A Non-blocking procedural assignment is scheduled to occur without blocking the procedural flow to subsequent statements.

# Nonblocking Statements are odd!

 

`a = 1;`

`b = a;`

`c = b;`

`a <= 1;`

`b <= a;`

`c <= b;`

Blocking assignment:

`a = b = c = 1`


Nonblocking assignment:

`a = 1`

`b = old value of a`

`c = old value of b`

# Nonblocking Looks Like Latches

 


- RHS of nonblocking taken from latches
- RHS of blocking taken from wires

`a = 1;`

`b = a;`

`c = b;`

“

 


`a <= 1;`


`b <= a;`

`c <= b;`

“

 

# Examples

 

- Blocking:  
always @(A1 or B1 or C1 or M1)  
begin  
    M1=#3(A1 & B1);  
    Y1= #1(M1|C1);  
end
- Non-Blocking:  
always @(A2 or B2 or C2 or M2)  
begin  
    M2<=#3(A2 & B2);  
    Y2<=#1(M1 | C1);  
end


Statement executed at time t causing M1 to be assigned at t+3

Statement executed at time t+3 causing Y1 to be assigned at time t+4

Statement executed at time t causing M2 to be assigned at t+3


Statement executed at time t causing Y2 to be assigned at time t+1.  
Uses old values.
 
# Order dependency of Concurrent Statements



- Order of concurrent statements does not affect how a synthesizer synthesizes a circuit.
- It can affect simulation results.
 
# Order dependency of Concurrent Statements



- always @(posedge clock)

```
begin: CONCURR_1
```

```
Y1<=A;
```


```
end
```

- always @(posedge clock)

```
begin: CONCURR_2
```

```
if(Y1) Y2=B; else Y2=0;
```


```
end
```

 

*Can you figure out the possible mismatch of simulation with synthesis results?*




# Explanation of the mismatch

 

- The actual circuit is a *concurrent* process.
- The first and second flip flop are operating parallel.
- However if the simulator simulates CONCURR\_1 block before CONCURR\_2, we have an error. Why?
- So, how do we solve the problem?


# Solution

 

- always @(posedge clock)  
begin  
    Y1<=A;  
    if(Y1==1)  
        Y2<=B;  
    else  
        Y2<=0;  
end

*With non-blocking assignments  
the order of the assignments  
is immaterial...*


# Parameterized Design

 

- ```
module vector_and(z, a, b);  
  parameter cardinality = 1;  
  input [cardinality-1:0] a, b;  
  output [cardinality-1:0] z;  
  wire [cardinality-1:0] z = a & b;  
endmodule
```
- We override these parameters when we instantiate the module as:  

```
module Four_and_gates(OutBus, InBusA, InBusB);  
  input [3:0] InBusA, InBusB; output[3:0] OutBus;  
  Vector_And #(4) My_And(OutBus, InBusA, InBusB);  
endmodule
```

# Functions (cont'd)

 


- Function Declaration and Invocation
  - Declaration syntax:

```
function <range_or_type> <func_name>;  
    <input_declaration(s)>  
    <variable_declaration(s)>  
    begin // if more than one statement needed  
        <statements>  
    end // if begin used  
endfunction
```

# Function Examples

## Controllable Shifter

 

```
module shifter;
`define LEFT_SHIFT      1'b0
`define RIGHT_SHIFT     1'b1
reg [31:0] addr, left_addr,
    right_addr;
reg control;
```

```
initial
begin
```

```
    ...
```

```
end
```


```
always @(addr)begin
    left_addr  =shift(addr,
    `LEFT_SHIFT);
    right_addr
    =shift(addr,`RIGHT_SHIFT);
```

```
end
```


```
function [31:0]shift;
input [31:0] address;
input control;
begin
    shift = (control==`LEFT_SHIFT)
    ?(address<<1) : (address>>1);
end
endfunction
```

```
endmodule
```


# How Are Simulators Used?

 

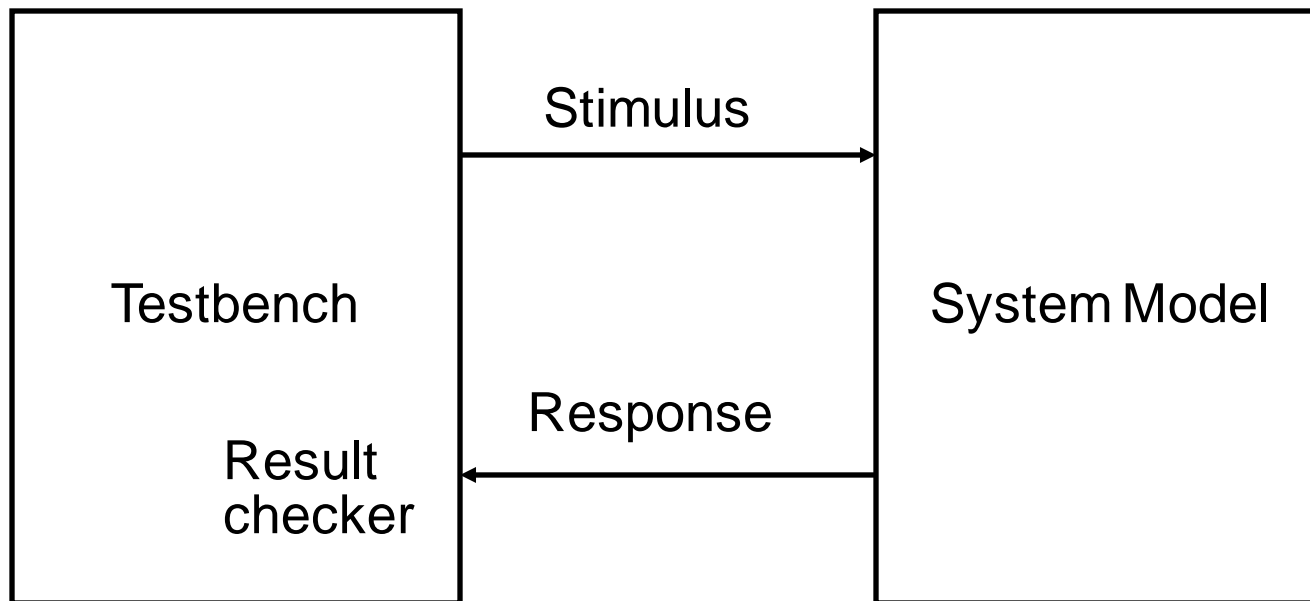- Testbench generates stimulus and checks response
- Coupled to model of the system
- Pair is run simultaneously



# Looking back at our multiplexer

 


- “Dataflow” Descriptions of Logic

```
//Dataflow description of mux
module mux2 (in0, in1, select, out);
    input in0,in1,select;
    output out;
    assign out = (~select & in0)
                | (select & in1);
endmodule // mux2
```

Alternative:

```
assign out = select ? in1 : in0;
```

# TestBench of the Multiplexer

 

- Testbench



```
module testmux;
  reg a, b, s;
  wire f;
  reg expected;

  mux2 myMux (.select(s), .in0(a), .in1(b), .out(f));


  initial
    begin
      s=0; a=0; b=1; expected=0;
      #10 a=1; b=0; expected=1;
      #10 s=1; a=0; b=1; expected=1;
    end
  initial
    $monitor(
      "select=%b in0=%b in1=%b out=%b, expected out=%b time=%d",
      s, a, b, f, expected, $time);
endmodule // testmux
```



# A Car Speed Controller

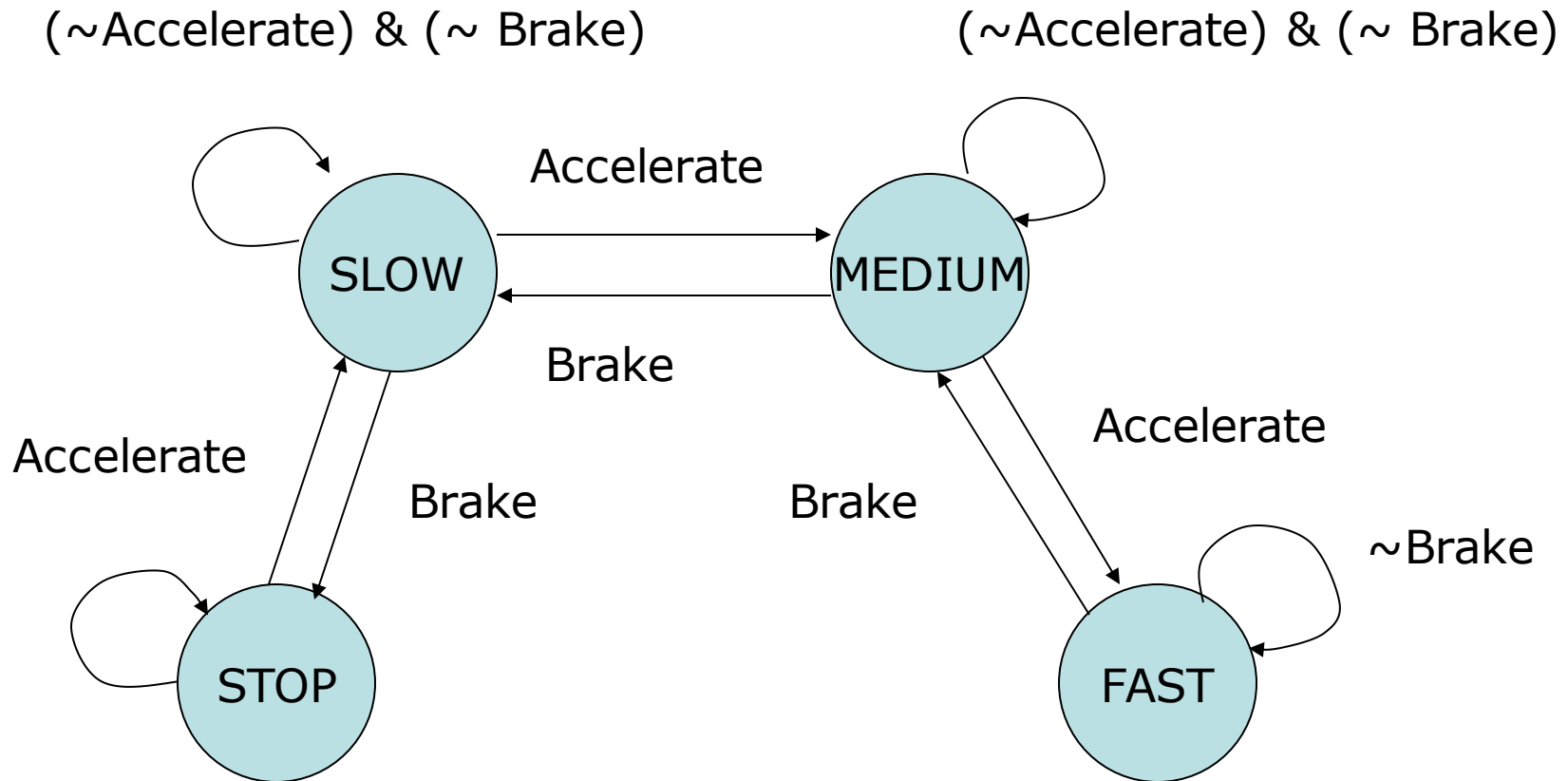 


# Car Controller Coding

 

```
module fsm_car_speed_1(clk, keys, brake, accelerate,
    speed);
    input clk, keys, brake, accelerate;
    output [1:0] speed;
    reg [1:0] speed;

    parameter stop    = 2'b00,
               slow   = 2'b01,
               mdium  = 2'b10,
               fast    = 2'b11;
```

# Car Controller (contd.)

 


```
always @(posedge clk or
        negedge keys)
begin
    if(!keys)
        speed = stop;
    else if(accelerate)
        case(speed)
            stop: speed = slow;
            slow: speed = mdium;
            mdium: speed = fast;
            fast: speed = fast;
        endcase
end
```

```
    else if(brake)
        case(speed)
            stop: speed = stop;
            slow: speed = stop;
            mdium: speed = slow;
            fast: speed = mdium;
        endcase
    else
        speed = speed;
    end
end
```

```
endmodule
```

# A Better Way!

 

- We keep a separate control part where the next state is calculated.
- The other part generates the output from the next state.
- We follow this architecture in the coding of any finite state machines, like ALU, etc. (to be discussed later)

```

module fsm_car_speed_2(clk, keys,
    brake, accelerate, speed);
    input clk, keys, brake, accelerate;
    output [1:0] speed;
    reg [1:0] speed;
    reg [1:0] newspeed;

```

```

    parameter stop  = 2'b00,
               slow  = 2'b01,
               mdium = 2'b10,
               fast  = 2'b11;

```

```

always @(keys or brake or
    accelerate or speed)

```

```

begin
    case(speed)
        stop:
            if(accelerate)
                newspeed = slow;

        else
            newspeed = stop;

```

```

    slow:
        if(brake)
            newspeed = stop;
        else if(accelerate)
            newspeed = mdium;
        else
            newspeed = slow;
    mdium:
        if(brake)
            newspeed = slow;
        else if(accelerate)
            newspeed = fast;
        else
            newspeed = mdium;
    fast:
        if(brake)
            newspeed = mdium;
        else
            newspeed = fast;
    default:
        newspeed = stop;
    endcase
end


```

```


always @(posedge clk or
    negedge keys)
begin
    if(!keys)
        speed = stop;
    else
        speed = newspeed;
end

endmodule

```

 
 
## Conclusion : Write codes which can be translated into hardware !



The following cannot be translated into hardware( non - synthesizable):

- Initial blocks
  - Used to set up initial state or describe finite testbench stimuli
  - Don't have obvious hardware component
- Delays
  - May be in the Verilog source, but are simply ignored
- In short, write codes with a hardware in your mind. In other words do not depend too much upon the tool to decide upon the resultant hardware.
- Finally, remember that you are a better designer than the tool.