

## Indian Institute of Technology (IIT-Kharagpur)

AUTUMN Semester, 2022

COMPUTER SCIENCE AND ENGINEERING

CS39001: Computer Organization Lab

Lab Test (Group 2)

**INSTRUCTIONS:** Please upload the verilog and project files to CSE Moodle.

You can submit the circuit diagrams on a sheet of paper. Make sure to write your name and roll number of the sheet.

Design a rotate circuit with shifters and adders only

**Objective of the Project:**

In this project, we would design a circuit which takes as input  $(x, y)$ , both of which can be represented by an 8-bit number, and an angle to rotate by  $\theta$ . The circuit should produce an output  $x_1, y_1$ , where the following holds:

$$\begin{pmatrix} x_1 \\ y_1 \end{pmatrix} = \frac{1}{\cos\theta} \begin{pmatrix} \cos\theta & -\sin\theta \\ \sin\theta & \cos\theta \end{pmatrix} \cdot \begin{pmatrix} x \\ y \end{pmatrix}$$

For your convenience we provide with a look-up which you can store in your design to look up the value of  $k = -\log_2(\tan\theta)$ . Note that this is not defined for  $\theta = 0^\circ$ . Also assume your possible values of  $\theta$  given in Table 1, along with an additional possible input of  $0^\circ$ .

For the design proceed in the following steps:

1. Represent  $x$  and  $y$  as two 8-bit numbers. Express  $x_1, y_1$  in terms of  $x$  and  $y$ , and  $k$ . Note that the transformations can be done with only an 8-bit adder, and some programmable shifters. You can use other associated peripheral data-path elements, but no multipliers, etc. Draw the circuit diagram. For  $\theta = 0^\circ$ ,  $x_1, y_1$  will be outputted unchanged. (20 marks)
2. Write the verilog code Rotbytheta in the Xilinx tool for realizing the circuit. Also write the test-bench to simulate the verilog code. Note that the top-level of the design module Rotbytheta must be structural, while the internal modules, may be behavioral. (20 marks)
3. Download the bit-stream onto your FPGA device and demonstrate its working. (10 marks)

Table 1: Different shift values ( $k$ ) for various  $\theta$ 

$\theta$	$10^\circ$	$20^\circ$	$30^\circ$	$40^\circ$	$60^\circ$	$70^\circ$	$80^\circ$
$k$	3	2	1	0	-1	-2	-3